

CO3-AT1

SIMULATION TASK

Using MATLAB/Scilab, design a quarter-wave transformer to match a $40\ \Omega$ load to a $75\ \Omega$ transmission line at $1.5\ \text{GHz}$. Determine the transformer characteristic impedance and physical length.

